

## Question No. 1

a)	$X = A \cdot (\bar{A} + \bar{B})$ $A \cdot \bar{A} \cdot \bar{B}$ $+$	[1] [1] [1]	3																				
b)	$X = A \cdot \bar{A} \bar{B}$ $X = A \cdot \bar{A} + A \cdot \bar{B}$ $= 0 + A \cdot \bar{B}$ $= A \cdot \bar{B}$	[1] [1] [1]	3																				
c)	logic circuit has: 1 AND gate and 1 NOT gate inputs to one NOT gate is B inputs to AND gate are A and output from NOT gate	[1] [1] [1]	3																				
d)	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>X</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	X	Y	0	0	0	0	0	1	0	1	1	0	0	1	1	1	1	0	[1] [1] [1] [1]	4
A	B	X	Y																				
0	0	0	0																				
0	1	0	1																				
1	0	0	1																				
1	1	1	0																				
e)	half adder	[1]	1																				

## Question No. 2

a) i)	Input		Output		1 mark for each correct column (A and B)	2
	X	Y	A	B		
	0	0	0	0		
	0	1	0	1		
	1	0	0	1		
	1	1	1	0		
a) ii)	Half adder					1
a) iii)	C // Carry S // Sum  represents the <u>carry part of the addition of two bits</u> represents the <u>sum part of the addition of two bits</u>					4
b) i)	A. (A.B + C)					2
b) ii)	Allow follow through from (b)(i)  A.(A.B+C) = A.A.B + A.C = A.B + A.C = A.(B+C)  1 mark for each correct simplification line – max 2 1 mark for A.(B+C) if correct answer to part (b)(i)					3

## Question No. 3

a) i)	Input			Working space	Output		1 mark each column  If zero marks then 6 or 7 pairs correct – 1 mark	2
	P	Q	R		J	K		
	0	0	0		0	0		
	0	0	1		0	1		
	0	1	0		0	1		
	0	1	1		1	0		
	1	0	0		0	1		
	1	0	1		1	0		
	1	1	0		1	0		
	1	1	1		1	1		
a) ii)	Full adder						1	
a) iii)	C / Carry S / Sum represents the carry part of the addition of three bits represents the sum part of the addition of three bits						4	
b) i)	A. (A+B).C						2	
b) ii)	Allow follow through from (b)(i)  A. ((A+B).C) = A.(A.C + B.C) = A.A.C + A.B.C = A.C + A.B.C = A.C (1 + B) = A.C.1 = A.C  1 mark for each correct simplification line – max 3 [3] 1 mark for A.C if correct answer to part (b)(i) [1]						4	

### Question No. 4

a)	NOR	1																									
b) i)	<div>1 mark for X column, 1 mark for Y column</div> <table><tr><th>A</th><th>B</th><th>Working Space</th><th>X</th><th>Y</th></tr><tr><td>0</td><td>0</td><td></td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td></td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td></td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td></td><td>1</td><td>0</td></tr></table>	A	B	Working Space	X	Y	0	0		0	0	0	1		0	1	1	0		0	1	1	1		1	0	2
A	B	Working Space	X	Y																							
0	0		0	0																							
0	1		0	1																							
1	0		0	1																							
1	1		1	0																							
b) ii)	Half adder	1																									
b) iii)	<div>1 mark per bullet</div> <div><input type="checkbox"/> X is (used for) <u>carry</u></div> <div><input type="checkbox"/> Y is (used for) <u>sum</u></div>	2																									

c)	<p><b>1 mark per bullet for working (max 4)</b></p> $\overline{A}.\overline{B}.\overline{C}.\overline{D} \sqcup \overline{A}.\overline{B}.\overline{C}.D \sqcup \overline{A}.\overline{B}.C.\overline{D} \sqcup \overline{A}.\overline{B}.C.D \sqcup \overline{A}.B.\overline{C}.\overline{D}$ $= \overline{A}.\overline{B}.\overline{C}.\overline{D} \sqcup \overline{A}.\overline{B}.\overline{C}.D \sqcup \overline{A}.\overline{B}.C.\overline{D} \sqcup \overline{A}.\overline{B}.C.D \sqcup \overline{A}.B.\overline{C}.\overline{D} \sqcup \overline{A}.B.\overline{C}.D$ <p>□ Adding in a second copy of the first term (Use of Idempotent Law)</p> $= \overline{A}.\overline{B}.[\overline{C}.\overline{D} \sqcup \overline{C}.D \sqcup C.\overline{D} \sqcup C.D] + \overline{A}.\overline{C}.\overline{D}.[B \sqcup \overline{B}]$ <p>□ Taking <math>\overline{A}.\overline{B}</math> and <math>\overline{A}.\overline{C}.\overline{D}</math> outside brackets (Associative Law)</p> $= \overline{A}.\overline{B}.[\overline{C}.\overline{D} \sqcup D \sqcup C.\overline{D} \sqcup D] + \overline{A}.\overline{C}.\overline{D}.[B \sqcup \overline{B}]$ <p>□ Grouping <math>\overline{C}.\overline{D} \sqcup D \sqcup C.\overline{D} \sqcup D</math> (Associative Law and Commutative Law)</p> $= \overline{A}.\overline{B}.[\overline{C}.\overline{D} \sqcup C.\overline{D} \sqcup D \sqcup D] + \overline{A}.\overline{C}.\overline{D}.[1]$ $= \overline{A}.\overline{B}.[\overline{C} \sqcup C] + \overline{A}.\overline{C}.\overline{D}.[1]$ $= \overline{A}.\overline{B}.[1] + \overline{A}.\overline{C}.\overline{D}.[1]$ <p>□ Replacing <math>[D \sqcup \overline{D}]</math> with 1 and replacing <math>[\overline{C} \sqcup C]</math> with 1 (Use of Complement Law)</p> $= \overline{A}.\overline{B} \sqcup \overline{A}.\overline{C}.\overline{D}$ <p>□ Reducing first four terms to <math>\overline{A}.\overline{B}</math> and reducing last two terms to <math>\overline{A}.\overline{C}.\overline{D}</math> (Use of Identity Law)</p> <p><b>1 mark for correct answer</b></p> $= \overline{A}.(\overline{B} \sqcup \overline{C}.\overline{D})$	5
----	--	---

### Question No. 5

a)	$X = ((P \text{ XOR } Q) \text{ XOR } R)$ $Y = ((P \text{ XOR } Q) \text{ AND } R) \text{ OR } (P \text{ AND } Q)$ or $X = (\overline{P.Q + P.Q}).R + (\overline{P.Q + P.Q}).\bar{R}$ $Y = (\overline{P.Q + P.Q}).R + P.Q$ <p><b>One</b> mark for correct use of XOR <b>One</b> mark for correct use of AND <b>One</b> mark for correct use of OR <b>One</b> mark for X correct <b>One</b> mark for Y correct</p>	5
b) i)	X: Sum Y: Carry (out)	2
b) ii)	Carry (in)	1

## Question No. 6

a)	<b>One</b> mark for working, (all three columns P, Q and R) <b>One</b> mark for each correct column Y, Z							3
	<b>A</b>	<b>B</b>	<b>C</b>	<b>P</b>	<b>Q</b>	<b>R</b>	<b>Y</b>	<b>Z</b>
	0	0	0	0	0	0	0	0
	0	0	1	0	0	0	1	0
	0	1	0	1	0	0	1	0
	0	1	1	1	0	1	0	1
	1	0	0	1	0	0	1	0
	1	0	1	1	0	1	0	1
	1	1	0	0	1	0	0	1
	1	1	1	0	1	0	1	1
b)	Full adder							1
c)	<b>One</b> mark for each point  $Y = \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} \bar{C} + A B C$ Purpose: Sum bit  $Z = \bar{A} B C + A \bar{B} C + A B \bar{C} + A B C$ Purpose: Carry output							4

### Question No. 7

a)	<p><b>One mark per bullet point to max 3</b></p> <ul style="list-style-type: none"><li>• Circuit / electronic components (construction)</li><li>• With <b>two states</b></li><li>• Used for data storage elements // memory</li><li>• ...to store 1 bit of data</li></ul>	3
b)	<p><b>One mark per bullet point to max 2</b></p> <ul style="list-style-type: none"><li>• SR flip-flop has undefined / invalid / indeterminate state // JK flip-flop is stable</li><li>• Description of undefined / invalid / indeterminate state for SR // Description of why JK flip flop is stable</li><li>• JK flip flop has a clock pulse</li></ul>	2



## Question No. 8

a)	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	1									
A	B	X																								
0	0	1																								
0	1	1																								
1	0	1																								
1	1	0																								
b) i)	<table><tr><th>S</th><th>R</th><th>Q</th><th><math>\overline{Q}</math></th></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr></table>	S	R	Q	$\overline{Q}$	1	0	0	1	1	1	0	1	0	1	1	0	1	1	1	0	0	0	1	1	4
S	R	Q	$\overline{Q}$																							
1	0	0	1																							
1	1	0	1																							
0	1	1	0																							
1	1	1	0																							
0	0	1	1																							
b) ii)	<p>S = 0 R = 0</p> <p>Produces <math>Q = 1</math> , <math>\overline{Q} = 1</math> // Q and <math>\overline{Q}</math> have same value But Q and <math>\overline{Q}</math> should be complements of each other Becomes unstable</p>	3																								
c) i)	Clock (pulse)	1																								
c) ii)	<p>All four possibilities are valid The 1-1 combination changes output to logical complement Unstable state avoided Invalid state cannot occur // the flip-flop is stable</p>	1																								
d)	<p>Memory // data storage Stores a single bit</p>	2																								

## Question No. 9

a)	<table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0	1																					
A	B	X																																				
0	0	1																																				
0	1	0																																				
1	0	0																																				
1	1	0																																				
b)	<table><tr><td></td><td>S</td><td>R</td><td>Q</td><td><math>\overline{Q}</math></td><td></td></tr><tr><td>Initially</td><td>1</td><td>0</td><td>1</td><td>0</td><td></td></tr><tr><td>S changed to 0</td><td>0</td><td>0</td><td>1</td><td>0</td><td>(1)</td></tr><tr><td>R changed to 1</td><td>0</td><td>1</td><td>0</td><td>1</td><td>(1)</td></tr><tr><td>R changed to 0</td><td>0</td><td>0</td><td>0</td><td>1</td><td>(1)</td></tr><tr><td>S and R changed to 1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>(1)</td></tr></table>		S	R	Q	$\overline{Q}$		Initially	1	0	1	0		S changed to 0	0	0	1	0	(1)	R changed to 1	0	1	0	1	(1)	R changed to 0	0	0	0	1	(1)	S and R changed to 1	1	1	0	0	(1)	4
	S	R	Q	$\overline{Q}$																																		
Initially	1	0	1	0																																		
S changed to 0	0	0	1	0	(1)																																	
R changed to 1	0	1	0	1	(1)																																	
R changed to 0	0	0	0	1	(1)																																	
S and R changed to 1	1	1	0	0	(1)																																	
c) i)	Clock (pulse)	1																																				
c) ii)	<p><b>Max 2 marks per problem – max 4 marks</b></p> <p><b>Problem 1</b></p> <ul style="list-style-type: none"><li>One combination of S and R gives NOT valid / indeterminate output // Q and <math>\overline{Q}</math> have the same value</li><li>The JK flip-flop does not allow for Q and <math>\overline{Q}</math> to have the same value for any combination of inputs // <math>\overline{Q}</math> and Q have to be complementary</li></ul> <p><b>Problem 2</b></p> <ul style="list-style-type: none"><li>Inputs may not arrive at the same time</li><li>The JK flip-flop has a clock pulse to synchronise inputs</li></ul>	4																																				

## Boolean Algebra and Logic Circuits

### Question No. 10

a) i)	<table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	1																																																																		
	A	B	X																																																																																
	0	0	1																																																																																
	0	1	1																																																																																
	1	0	1																																																																																
1	1	0																																																																																	
a) ii)	<table><tr><td>A</td><td>B</td><td>C</td><td>X</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	X	0	0	0	1	0	0	1	1	0	1	0	1	0	1	1	1	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	1																																													
	A	B	C	X																																																																															
	0	0	0	1																																																																															
	0	0	1	1																																																																															
	0	1	0	1																																																																															
	0	1	1	1																																																																															
	1	0	0	1																																																																															
	1	0	1	1																																																																															
	1	1	0	1																																																																															
1	1	1	0																																																																																
b) i)	<table><tr><td></td><td>S</td><td>R</td><td>Q</td><td><math>\overline{Q}</math></td><td></td></tr><tr><td>Initially</td><td>1</td><td>0</td><td>0</td><td>1</td><td></td></tr><tr><td>R changed to 1</td><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>S changed to 0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>S changed to 1</td><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>S and R changed to 0</td><td>0</td><td>0</td><td>1</td><td>1</td><td></td></tr></table>		S	R	Q	$\overline{Q}$		Initially	1	0	0	1		R changed to 1	1	1	0	1	1	S changed to 0	0	1	1	0	1	S changed to 1	1	1	1	0	1	S and R changed to 0	0	0	1	1		3																																													
		S	R	Q	$\overline{Q}$																																																																														
	Initially	1	0	0	1																																																																														
	R changed to 1	1	1	0	1	1																																																																													
	S changed to 0	0	1	1	0	1																																																																													
	S changed to 1	1	1	1	0	1																																																																													
S and R changed to 0	0	0	1	1																																																																															
b) ii)	<div><input type="checkbox"/> Q and <math>\overline{Q}</math> have same value</div> <div><input type="checkbox"/> Q and <math>\overline{Q}</math> should be complements of each other</div> <div><input type="checkbox"/> Flip-flop becomes unstable</div> <div>1 mark for each point, max 2</div>					2																																																																													
	c) i)	<table><tr><td></td><td></td><td></td><td rowspan="2">Working space</td><td colspan="2">Initial values</td><td colspan="2">Final values</td></tr><tr><td>J</td><td>K</td><td>Clock</td><td>Q</td><td><math>\overline{Q}</math></td><td>Q</td><td><math>\overline{Q}</math></td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td><td>1</td><td>1</td><td>0</td></tr></table>					Working space	Initial values		Final values		J	K	Clock	Q	$\overline{Q}$	Q	$\overline{Q}$	0	0	1		1	0	1	0	0	0	1		0	1	0	1	0	1	1		1	0	0	1	0	1	1		0	1	0	1	1	0	1		1	0	1	0	1	0	1		0	1	1	0	1	1	1		1	0	0	1	1	1	1		0	1	1	0	4
					Working space			Initial values		Final values																																																																									
J		K	Clock	Q		$\overline{Q}$	Q	$\overline{Q}$																																																																											
0		0	1		1	0	1	0																																																																											
0		0	1		0	1	0	1																																																																											
0		1	1		1	0	0	1																																																																											
0		1	1		0	1	0	1																																																																											
1		0	1		1	0	1	0																																																																											
1		0	1		0	1	1	0																																																																											
1	1	1		1	0	0	1																																																																												
1	1	1		0	1	1	0																																																																												
1 mark per shaded row																																																																																			

c) ii)	<ul style="list-style-type: none"><li><input type="checkbox"/> S-R flip-flop has an invalid combination of S and R // The S_R flip flop allows both Q and <math>\bar{Q}</math> to have the same value // S-R flip-flop inputs may arrive at different times 1</li><li><input type="checkbox"/> The J-K flip-flop does not allow for Q and <math>\bar{Q}</math> to have the same value // All four combination of values for J and K are valid // J-K flip-flop incorporates a clock pulse for synchronisation 1</li></ul>	2
d)	<ul style="list-style-type: none"><li><input type="checkbox"/> A flip-flop can store either a 0 or a 1</li><li><input type="checkbox"/> Computers use bits to store data</li><li><input type="checkbox"/> Flip-flops can therefore be used to store bits (of data)</li><li><input type="checkbox"/> Memory can be created from flip-flops</li></ul> <p>1 mark for valid point, max 2</p>	2

### Question No. 11

-	(logic) Circuit // bi-stable Two Memory // data storage // registers // storing one bit of data JK/SR/D/T SR/JK/T/D	5
---	---	---

## Question No. 12

a) i)	<table> <tr> <th colspan="3">Circuit 1</th></tr> <tr> <th>A</th><th>B</th><th>X</th></tr> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </table>	Circuit 1			A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	1
Circuit 1																				
A	B	X																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
a) ii)	<table> <tr> <th colspan="3">Circuit 2</th></tr> <tr> <th>A</th><th>B</th><th>X</th></tr> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </table>	Circuit 2			A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	1
Circuit 2																				
A	B	X																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
b) i)	<ul style="list-style-type: none"> <li>circuit 1: <math>\overline{A.B}</math></li> <li>circuit 2: <math>\overline{A} + \overline{B}</math></li> </ul>	2																		
b) ii)	$\overline{A.B} \equiv \overline{A} + \overline{B}$	1																		
c)	$\overline{\overline{(A+B).B}}$ Mark as follows: $\overline{(A+B)}$ $.B$ bar over whole expression	3																		
d)	$\overline{\overline{(A+B).B}}$ $= \overline{\overline{(A+B)} + \overline{B}}$ $= (A+B) + \overline{B}$ $= A + (B + \overline{B})$ $= A + 1$ $= 1$ allow f.t. from (c)	3																		

## Question No. 13

a) i)		Circuit 1			1
		A	B	X	
		0	0	1	
		0	1	0	
		1	0	0	
		1	1	0	
a) ii)		Circuit 2			1
		A	B	X	
		0	0	1	
		0	1	0	
		1	0	0	
		1	1	0	
b) i)	circuit 1 $\overline{A+B}$ circuit 2 $\overline{A} \cdot \overline{B}$				2
b) ii)	$\overline{A+B} \equiv \overline{A} \cdot \overline{B}$				1
c)	$\overline{\overline{(A.B)} + B}$ mark as : $\overline{(A.B)}$ $+ B$ bar over whole expression				3
d)	$\overline{\overline{(A.B)} + B}$ $= \overline{\overline{(A.B)}} \cdot \overline{B}$ $= (A.B) \cdot \overline{B}$ $= A \cdot (\overline{B.B})$ $= A \cdot 0$ $= 0$ allow f.t. from (c)				3

## Question No. 14

a) i)	$\overline{A}.B.C + A.B.\overline{C} + A.B.C$	3																									
a) ii)	<div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td></tr></table> <div>C</div>		00	01	11	10	0	0	0	1	0	1	0	1	1	0	1										
	00	01	11	10																							
0	0	0	1	0																							
1	0	1	1	0																							
a) iii)	<div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td></tr></table> <div>C</div> <div>1 mark for each loop</div> <div>Allow f.t. from (ii)</div>		00	01	11	10	0	0	0	1	0	1	0	1	1	0	2										
	00	01	11	10																							
0	0	0	1	0																							
1	0	1	1	0																							
a) iv)	$X = A.B + B.C$ <div>Allow f.t. from (iii)</div>	2																									
b) i)	<div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>10</td><td>0</td><td>1</td><td>1</td><td>0</td></tr></table> <div>CD</div> <div>1 mark row headings</div> <div>1 mark column headings</div> <div>1 mark per 2 correct rows (based on headings)</div>		00	01	11	10	00	0	1	1	0	01	0	0	0	0	11	0	0	1	0	10	0	1	1	0	4
	00	01	11	10																							
00	0	1	1	0																							
01	0	0	0	0																							
11	0	0	1	0																							
10	0	1	1	0																							



b) ii)	<div><div><div>AB</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>10</td><td>0</td><td>1</td><td>1</td><td>0</td></tr></table><div>CD</div></div><div><p>1 mark for loop with two 1s</p><p>1 mark for looping the four 1s</p></div></div>		00	01	11	10	00	0	1	1	0	01	0	0	0	0	11	0	0	1	0	10	0	1	1	0	2
	00	01	11	10																							
00	0	1	1	0																							
01	0	0	0	0																							
11	0	0	1	0																							
10	0	1	1	0																							
b) iii)	<div><div>X =</div><div><div>B.<math>\overline{D}</math></div><div>+ A.B.C</div></div></div>	2																									

## Question No. 15

a) i)	$Z = P \cdot \overline{Q} \cdot \overline{R} + P \cdot \overline{Q} \cdot R + P \cdot Q \cdot R$	3																									
a) ii)	<p style="text-align: center;">PQ</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>R 0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>R 1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr></table>		00	01	11	10	R 0	0	0	0	1	R 1	0	0	1	1	1										
	00	01	11	10																							
R 0	0	0	0	1																							
R 1	0	0	1	1																							
a) iii)	<p>1 mark each loop</p> <p style="text-align: center;">PQ</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>R 0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>R 1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr></table> <p>Allow f.t. from (ii)</p>		00	01	11	10	R 0	0	0	0	1	R 1	0	0	1	1	2										
	00	01	11	10																							
R 0	0	0	0	1																							
R 1	0	0	1	1																							
a) iv)	$Z = P \cdot \overline{Q} + P \cdot R$ <p>Allow f.t. from (iii)</p>	1																									
b) i)	<p>1 mark row headings. 1 mark column headings. 1 mark per 2 correct rows (based on headings)</p> <p style="text-align: center;">PQ</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>01</td><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>11</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>10</td><td>0</td><td>0</td><td>0</td><td>0</td></tr></table>		00	01	11	10	00	0	0	0	0	01	0	1	1	1	11	0	1	1	0	10	0	0	0	0	4
	00	01	11	10																							
00	0	0	0	0																							
01	0	1	1	1																							
11	0	1	1	0																							
10	0	0	0	0																							

b) ii)	<p>1 mark for loop with two 1s; 1 mark for loop with four 1s</p> <p style="text-align: center;"><b>PQ</b></p> <table border="1"><tr><td></td><td><b>00</b></td><td><b>01</b></td><td><b>11</b></td><td><b>10</b></td></tr><tr><td><b>00</b></td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td><b>01</b></td><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td><b>11</b></td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td><b>10</b></td><td>0</td><td>0</td><td>0</td><td>0</td></tr></table> <p>RS</p> <p>Allow f.t. from (i) -1 for each incorrect grouping, max. 2 errors</p>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>	<b>00</b>	0	0	0	0	<b>01</b>	0	1	1	1	<b>11</b>	0	1	1	0	<b>10</b>	0	0	0	0	2
		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>																						
<b>00</b>	0	0	0	0																							
<b>01</b>	0	1	1	1																							
<b>11</b>	0	1	1	0																							
<b>10</b>	0	0	0	0																							
b) iii)	<p><math display="block">Z = Q.S + P.R.\bar{S}</math></p> <p>Allow f.t. from (ii). -1 error if more than 2 terms</p>	2																									

## Question No. 16

a)	$S = ( \overline{P} + (\overline{Q+R}) ) \cdot R$ $\overline{P}$ $(\overline{Q+R})$ $(\overline{P} + (\overline{Q+R}) )$ $\cdot R \quad \text{(must be outside final brackets)}$ Or $\overline{P}$ $(\overline{Q+R})$ $\overline{P} + (\overline{Q+R})$ $(\text{.....}) \cdot R$	1 1 1 1  1 1 1 1	4																																													
b)	<table><tr><th>P</th><th>Q</th><th>R</th><th>Working space</th><th>S</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table> <p>2 marks all correct, 1 mark seven correct, 0 marks six or fewer correct</p>	P	Q	R	Working space	S	0	0	0		0	0	0	1		1	0	1	0		0	0	1	1		1	1	0	0		0	1	0	1		0	1	1	0		0	1	1	1		0		2
P	Q	R	Working space	S																																												
0	0	0		0																																												
0	0	1		1																																												
0	1	0		0																																												
0	1	1		1																																												
1	0	0		0																																												
1	0	1		0																																												
1	1	0		0																																												
1	1	1		0																																												
c) i)	<p style="text-align: center;"><b>PQ</b></p> <table><tr><td></td><td><b>00</b></td><td><b>01</b></td><td><b>11</b></td><td><b>10</b></td></tr><tr><td><b>R</b> 0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td></tr></table>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>	<b>R</b> 0	0	0	0	0	1	1	1	0	0		1																														
	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>																																												
<b>R</b> 0	0	0	0	0																																												
1	1	1	0	0																																												
c) ii)	<p style="text-align: center;"><b>PQ</b></p> <table><tr><td></td><td><b>00</b></td><td><b>01</b></td><td><b>11</b></td><td><b>10</b></td></tr><tr><td><b>R</b> 0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td></tr></table>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>	<b>R</b> 0	0	0	0	0	1	1	1	0	0		1																														
	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>																																												
<b>R</b> 0	0	0	0	0																																												
1	1	1	0	0																																												

c) iii)	$S = \bar{P} \cdot R$	1
d)	$S = (\bar{P} + (\bar{Q} + \bar{R})) \cdot R$ $S = (\bar{P} + (\bar{Q} \cdot \bar{R})) \cdot R \quad // \quad \bar{P} \cdot R + (\bar{Q} + \bar{R}) \cdot R$ $S = (\bar{P} \cdot R) + (\bar{Q} \cdot \bar{R} \cdot R)$ $S = \bar{P} \cdot R + \bar{Q} \cdot 0$ $S = \bar{P} \cdot R + 0$ $S = \bar{P} \cdot R$	 1 1 ) ) 1

## Question No. 17

a)	$X = A.(\overline{B} + (B . C))$ $B.C$ $\overline{B} + B.C$ $A.$	1 1 1	3																																													
b)	<table><tr><th>A</th><th>B</th><th>C</th><th>Working Space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table> <p>1 mark first four entries, 1 mark for the last four entries</p>	A	B	C	Working Space	X	0	0	0		0	0	0	1		0	0	1	0		0	0	1	1		0	1	0	0		1	1	0	1		1	1	1	0		0	1	1	1		1		2
A	B	C	Working Space	X																																												
0	0	0		0																																												
0	0	1		0																																												
0	1	0		0																																												
0	1	1		0																																												
1	0	0		1																																												
1	0	1		1																																												
1	1	0		0																																												
1	1	1		1																																												
c) i)	<table><tr><td colspan="2"></td><td colspan="4">AB</td></tr><tr><td colspan="2"></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td rowspan="2">C</td><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr></table>			AB						00	01	11	10	C	0	0	0	0	1	1	0	0	1	1		1																						
		AB																																														
		00	01	11	10																																											
C	0	0	0	0	1																																											
	1	0	0	1	1																																											
c) ii)	<table><tr><td colspan="2"></td><td colspan="4">AB</td></tr><tr><td colspan="2"></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td rowspan="2">C</td><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr></table>			AB						00	01	11	10	C	0	0	0	0	1	1	0	0	1	1		2																						
		AB																																														
		00	01	11	10																																											
C	0	0	0	0	1																																											
	1	0	0	1	1																																											
c) iii)	$X = A.\overline{B} + A.C$  1      1		2																																													
d)	$X = A.(\overline{B} + (B . C))$ $X = A.(\overline{B} + C)$ $X = A.\overline{B} + A.C$	1 1 (dependent mark – must be correct outcome from previous line)	2																																													

## Question No. 18

a) i)	2 marks all products correct, 1 mark 2 or 3 products correct $X = \bar{A}.B.\bar{C} + \bar{A}.B.C + A.\bar{B}.\bar{C} + A.\bar{B}.C$	2																									
a) ii)	1 mark for all correct bits <div><div><div></div><div></div><div><b>C</b></div></div><div><div></div><div></div><div></div><div><b>AB</b></div></div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr></table></div>		00	01	11	10	0	0	1	0	1	1	0	1	0	1	1										
	00	01	11	10																							
0	0	1	0	1																							
1	0	1	0	1																							
a) iii)	1 mark for each correct loop <div><div><div></div><div></div><div><b>C</b></div></div><div><div></div><div></div><div></div><div><b>AB</b></div></div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr></table></div>		00	01	11	10	0	0	1	0	1	1	0	1	0	1	2										
	00	01	11	10																							
0	0	1	0	1																							
1	0	1	0	1																							
a) iv)	1 mark per bullet – allow follow through from 4(a)(iii) <ul style="list-style-type: none"><li><math>\bar{A}.B</math></li><li><math>+A.\bar{B}</math></li></ul> $X = \bar{A}.B + A.\bar{B}$	2																									
b) i)	1 mark per bullet max 2 <ul style="list-style-type: none"><li>Correct column headings and row headings – values only</li><li>Correct column headings and row headings – order</li></ul> 1 mark for 2 correct rows/columns, 2 marks for 4 correct rows/columns (based on headings) max 2 <div><div><div></div><div></div><div></div><div><b>CD</b></div></div><div><div></div><div></div><div></div><div><b>AB</b></div></div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>11</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>10</td><td>0</td><td>1</td><td>0</td><td>0</td></tr></table></div>		00	01	11	10	00	0	1	1	0	01	0	1	1	0	11	0	1	0	0	10	0	1	0	0	4
	00	01	11	10																							
00	0	1	1	0																							
01	0	1	1	0																							
11	0	1	0	0																							
10	0	1	0	0																							

b) ii)	<div>1 mark for each correct loop</div> <div><div>CD</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>11</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>10</td><td>0</td><td>1</td><td>0</td><td>0</td></tr></table></div>		00	01	11	10	00	0	1	1	0	01	0	1	1	0	11	0	1	0	0	10	0	1	0	0	2
	00	01	11	10																							
00	0	1	1	0																							
01	0	1	1	0																							
11	0	1	0	0																							
10	0	1	0	0																							
b) iii)	<div>1 mark per bullet</div> <div><math>\bar{A}.B</math> <math>+B.\bar{C}</math> <math>X = \bar{A}.B + B.\bar{C}</math></div>	2																									



## Question No. 19

a) i)	1 mark for 2 or 3 correct, 2 marks for 4 correct $X = \bar{A}.B.C + A.\bar{B}.C + A.B.\bar{C} + A.B.C$	2															
a) ii)	1 mark for the correct K-map <div style="text-align: center;"><b>AB</b></div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td><b>C</b> 0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table>		00	01	11	10	<b>C</b> 0	0	0	1	0	1	0	1	1	1	1
	00	01	11	10													
<b>C</b> 0	0	0	1	0													
1	0	1	1	1													
a) iii)	1 mark for each loop max 3 <div style="text-align: center;"><b>AB</b></div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td><b>C</b> 0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table>		00	01	11	10	<b>C</b> 0	0	0	1	0	1	0	1	1	1	2
	00	01	11	10													
<b>C</b> 0	0	0	1	0													
1	0	1	1	1													
a) iv)	1 mark for each pair. Allow follow through from (iii) <ul style="list-style-type: none"><li>• A.B</li><li>• +B.C</li><li>• +A.C</li></ul> $X = A.B + B.C + A.C$	2															

b) i)	<p>1 mark per bullet point max 2:</p> <ul style="list-style-type: none"><li>• Correct column headings and row headings – values only</li><li>• Correct column headings and row headings – order</li></ul> <p>1 mark for 2 correct rows or columns, 2 marks for 4 correct rows or columns (based on headings)</p> <table><tr><td colspan="2" rowspan="2"></td><th colspan="4">AB</th></tr><tr><th>00</th><th>01</th><th>11</th><th>10</th></tr><tr><th rowspan="4">CD</th><th>00</th><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><th>01</th><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><th>11</th><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><th>10</th><td>0</td><td>0</td><td>1</td><td>0</td></tr></table>			AB				00	01	11	10	CD	00	0	1	1	0	01	0	0	1	0	11	0	0	1	0	10	0	0	1	0	4
				AB																													
		00	01	11	10																												
CD	00	0	1	1	0																												
	01	0	0	1	0																												
	11	0	0	1	0																												
	10	0	0	1	0																												
b) ii)	<p>1 mark per loop</p> <table><tr><td colspan="2" rowspan="2"></td><th colspan="4">AB</th></tr><tr><th>00</th><th>01</th><th>11</th><th>10</th></tr><tr><th rowspan="4">CD</th><th>00</th><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><th>01</th><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><th>11</th><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><th>10</th><td>0</td><td>0</td><td>1</td><td>0</td></tr></table>			AB				00	01	11	10	CD	00	0	1	1	0	01	0	0	1	0	11	0	0	1	0	10	0	0	1	0	2
				AB																													
		00	01	11	10																												
CD	00	0	1	1	0																												
	01	0	0	1	0																												
	11	0	0	1	0																												
	10	0	0	1	0																												
b) iii)	<p>1 mark per bullet point:</p> <ul style="list-style-type: none"><li>• <math>A.B</math></li><li>• <math>+B.\bar{C}.\bar{D}</math></li></ul> <p><math>X = A.B + B.\bar{C}.\bar{D}</math></p>	2																															

## Question No. 20

a)	<p>1 mark per bullet point to max 3:</p> <ul style="list-style-type: none"><li>• Correct use of Idempotent law <math>Y = Y.Y</math> <math>Y = Y + Y</math></li><li>• Correct use of Complement law <math>0 = Y.\bar{Y}</math> <math>1 = Y + \bar{Y}</math></li><li>• Correct use of Distributive law <math>X(Y + Z) = X.Y + X.Z</math></li><li>• Correct use of Redundancy law <math>X\bar{Y} + Y = X + Y</math></li><li>• Correct use of identity law <math>X.1 = X</math></li></ul> <p>1 mark for the correct answer</p> <p>For example:</p> <p><math>X = A\bar{B}\bar{C} + AB\bar{C} + A.B.C</math> Idempotent law</p> <p><math>X = A\bar{B}\bar{C} + AB\bar{C} + AB\bar{C} + A.B.C</math> Distributive law</p> <p><math>X = A.\bar{C}.(\bar{B} + B) + A.B.(\bar{C} + C)</math> Complement/Inverse law</p> <p><math>X = A.\bar{C} + A.B</math></p> <p><math>X = A.(\bar{C} + B)</math> Correct answer</p> <p><math>X = A\bar{B}\bar{C} + AB\bar{C} + A.B.C</math> Distributive law</p> <p><math>X = A.\bar{C}.(\bar{B} + B) + A.B.C</math> Complement/Inverse law</p> <p><math>X = A.\bar{C} + A.B.C</math></p> <p><math>X = A.(\bar{C} + B.C)</math> Redundancy Law</p> <p><math>X = A.(\bar{C} + B)</math> Correct answer</p>	4																																				
b) i)	<p>1 mark for first four as 0, 1 mark for 1011</p> <table><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td></tr></table> <p>1 mark</p> <p>1 mark</p>	A	B	C	X	0	0	0	0	0	0	1	0	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	0	1	1	0	1	1	1	1	1	2
A	B	C	X																																			
0	0	0	0																																			
0	0	1	0																																			
0	1	0	0																																			
0	1	1	0																																			
1	0	0	1																																			
1	0	1	0																																			
1	1	0	1																																			
1	1	1	1																																			
b) ii)	<p>1 mark for correct K-map</p> <p>AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table> <p>C</p>		00	01	11	10	0	0	0	1	1	1	0	0	1	0	1																					
	00	01	11	10																																		
0	0	0	1	1																																		
1	0	0	1	0																																		
b) iii)	<p>1 mark for each correct loop to max 2</p> <p>AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table> <p>C</p>		00	01	11	10	0	0	0	1	1	1	0	0	1	0	2																					
	00	01	11	10																																		
0	0	0	1	1																																		
1	0	0	1	0																																		
b) iv)	<p>1 mark per bullet point:</p> <ul style="list-style-type: none"><li>• <math>A.\bar{C}</math></li><li>• <math>+ A.B</math></li></ul> <p><math>X = A.\bar{C} + A.B</math></p>	2																																				

## Question No. 21

a) i)	<div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table> <div>C</div>		00	01	11	10	0	1	1	0	1	1	1	1	0	1	1										
	00	01	11	10																							
0	1	1	0	1																							
1	1	1	0	1																							
a) ii)	<div>1 mark for each correct loop</div> <div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table> <div>C</div>		00	01	11	10	0	1	1	0	1	1	1	1	0	1	2										
	00	01	11	10																							
0	1	1	0	1																							
1	1	1	0	1																							
a) iii)	<div>1 mark per bullet point</div> <div><input type="checkbox"/> <math>\overline{A}</math></div> <div><input type="checkbox"/> <math>\overline{B}</math></div> <div><math>X = \overline{A} \square \overline{B}</math></div>	2																									
b) i)	<div>1 mark correct values and order of row and column headings</div> <div>3 marks fully correct table entries (based on headings) or</div> <div>2 marks table entries contain one error (based on headings) or</div> <div>1 mark table entries contain two errors (based on headings)</div> <div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>11</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>10</td><td>1</td><td>1</td><td>0</td><td>0</td></tr></table> <div>CD</div>		00	01	11	10	00	0	0	1	1	01	0	0	1	1	11	1	1	0	0	10	1	1	0	0	4
	00	01	11	10																							
00	0	0	1	1																							
01	0	0	1	1																							
11	1	1	0	0																							
10	1	1	0	0																							

b) ii)	<p>1 mark per loop</p> <p style="text-align: center;"><b>AB</b></p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td><b>CD</b> 00</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>11</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>10</td><td>1</td><td>1</td><td>0</td><td>0</td></tr></table>		00	01	11	10	<b>CD</b> 00	0	0	1	1	01	0	0	1	1	11	1	1	0	0	10	1	1	0	0	2
	00	01	11	10																							
<b>CD</b> 00	0	0	1	1																							
01	0	0	1	1																							
11	1	1	0	0																							
10	1	1	0	0																							
b) iii)	<p>1 mark for each bullet point</p> <ul style="list-style-type: none"><li><input type="checkbox"/> <math>\overline{A}.C</math></li><li><input type="checkbox"/> <math>+ A.\overline{C}</math></li></ul> <p><math>X = \overline{A}.C + A.\overline{C}</math></p>	2																									


## Question No. 22

a)	<p>1 mark for 3 or 4 correct products 2 marks for all 5 correct products</p> $X = \bar{A}.\bar{B}.\bar{C} + \bar{A}.\bar{B}.C + \bar{A}.B.C + A.\bar{B}.C + A.B.C$	2															
b)	<p>1 mark for correct answer</p> <p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>C</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td></td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table>		00	01	11	10	C	0	1	0	0		1	1	1	1	1
	00	01	11	10													
C	0	1	0	0													
	1	1	1	1													
c)	<p>1 mark per correct loop</p> <p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>C</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td></td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table>		00	01	11	10	C	0	1	0	0		1	1	1	1	2
	00	01	11	10													
C	0	1	0	0													
	1	1	1	1													
d)	<p>1 mark per bullet point.</p> <ul style="list-style-type: none"><li><math>\bar{A}.\bar{B}</math></li><li><math>+C</math></li></ul> $X = \bar{A}.\bar{B} + C \text{ // } X = C + \bar{A}.\bar{B}$	2															

## Question No. 23

a) i)	1 mark for each 2 correct products, i.e. 3 marks for 6, 2 marks for 4 or 5, 1 mark for 2 or 3 $X = \overline{A}.\overline{B}.\overline{C} + \overline{A}.\overline{B}.C + \overline{A}.B.\overline{C} + \overline{A}.B.C + A.\overline{B}.\overline{C} + A.\overline{B}.C$	3																							
a) ii)	1 mark for the correct K-map <table><tr><td></td><td></td><td colspan="4">AB</td></tr><tr><td></td><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td rowspan="2">C</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table>			AB						00	01	11	10	C	0	1	1	0	1	1	1	1	0	1	1
		AB																							
		00	01	11	10																				
C	0	1	1	0	1																				
	1	1	1	0	1																				
a) iii)	1 mark for each correct loop <table><tr><td></td><td></td><td colspan="4">AB</td></tr><tr><td></td><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td rowspan="2">C</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table>			AB						00	01	11	10	C	0	1	1	0	1	1	1	1	0	1	2
		AB																							
		00	01	11	10																				
C	0	1	1	0	1																				
	1	1	1	0	1																				
a) iv)	1 mark per bullet point: <ul style="list-style-type: none"><li>• <math>\overline{A}</math></li><li>• <math>+ \overline{B}</math></li></ul> $X = \overline{A} + \overline{B} // X = \overline{B} + \overline{A}$	2																							
b)	$X = ((\overline{W} + X).(Y + \overline{Z}))$ <p>One mark for correct use of <u>De Morgan's law</u> to +</p> <ul style="list-style-type: none"><li>• <math>X = (\overline{W} + X) + (Y + \overline{Z})</math></li></ul> <p>One mark for correct use of <u>De Morgan's law</u> + to</p> <ul style="list-style-type: none"><li>• <math>X = \overline{\overline{W}.X} + \overline{Y.Z}</math></li></ul> <p>One mark for correct answer</p> <ul style="list-style-type: none"><li>• <math>X = W.\overline{X} + \overline{Y}.Z</math></li></ul>	3																							

## Question No. 24

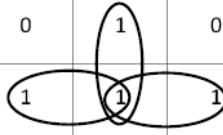a)	<p>For each expression, 2 marks all products correct no incorrect products seen, 1 mark 2 or 3 products correct, max 4</p> $X = \overline{A}.\overline{B}.C + \overline{A}.B.\overline{C} + A.\overline{B}.\overline{C} + A.B.C$ $Y = \overline{A}.B.C + A.\overline{B}.C + A.B.\overline{C} + A.B.C$	4																														
b)	<p>One mark for each correct K-map max 2</p> <div><div><p>OUTPUT X AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr></table></div><div><p>OUTPUT Y AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table></div></div>		00	01	11	10	0	0	1	0	1	1	1	0	1	0		00	01	11	10	0	0	0	1	0	1	0	1	1	1	2
	00	01	11	10																												
0	0	1	0	1																												
1	1	0	1	0																												
	00	01	11	10																												
0	0	0	1	0																												
1	0	1	1	1																												
c) i)	<p>One mark for OUTPUT X no loops OUTPUT Y one mark vertical loop correct one mark horizontal loops correct</p> <div><div><p>OUTPUT X AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr></table></div><div><p>OUTPUT Y AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table></div></div>		00	01	11	10	0	0	1	0	1	1	1	0	1	0		00	01	11	10	0	0	0	1	0	1	0	1	1	1	3
	00	01	11	10																												
0	0	1	0	1																												
1	1	0	1	0																												
	00	01	11	10																												
0	0	0	1	0																												
1	0	1	1	1																												
c) ii)	<p>One mark for each correct product and no incorrect products max 3</p> $A.B + B.C + A.C$	3																														
d)	<p>Logic circuit: Full Adder X: Sum Y: Carry</p>	3																														



## Question No. 25

a)	For X 1 mark for all products correct For Y 2 marks for 3 products correct, no other products seen $X = \bar{A}.\bar{B}.\bar{C} + A.B.C$ $Y = \bar{A}.B.C + A.\bar{B}.C + A.B.C$	3																														
b)	<p>One mark for each correct K-map max 2</p> <div><div><p>OUTPUT X AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table></div><div><p>OUTPUT Y AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table></div></div>		00	01	11	10	0	1	0	0	0	1	0	0	1	0		00	01	11	10	0	0	0	0	0	0	0	1	1	1	2
	00	01	11	10																												
0	1	0	0	0																												
1	0	0	1	0																												
	00	01	11	10																												
0	0	0	0	0																												
0	0	1	1	1																												
c) i)	<p>One mark for OUTPUT X no loops One mark for OUTPUT Y all loops correct and no others max 2</p> <div><div><p>OUTPUT X AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table></div><div><p>OUTPUT Y AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table></div></div>		00	01	11	10	0	1	0	0	0	1	0	0	1	0		00	01	11	10	0	0	0	0	0	0	0	1	1	1	2
	00	01	11	10																												
0	1	0	0	0																												
1	0	0	1	0																												
	00	01	11	10																												
0	0	0	0	0																												
0	0	1	1	1																												
c) ii)	One mark for each correct product $A.C + B.C$	2																														

## Question No. 26

a) i)	<b>One</b> mark for 2 correct, <b>two</b> marks for 4 correct and no other terms $X = \bar{P}.\bar{Q}.\bar{R}.\bar{S} + \bar{P}.\bar{Q}.R.\bar{S} + P.Q.\bar{R}.S + P.Q.R.S$	2																									
a) ii)	<b>Two marks</b> for fully correct K-map <b>One mark</b> for a K-map with one error <b>Zero marks</b> for a K-map with <b>two or more errors</b> <div><div>PQ</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>10</td><td>1</td><td>0</td><td>0</td><td>0</td></tr></table></div>		00	01	11	10	00	1	0	0	0	01	0	0	1	0	11	0	0	1	0	10	1	0	0	0	2
	00	01	11	10																							
00	1	0	0	0																							
01	0	0	1	0																							
11	0	0	1	0																							
10	1	0	0	0																							
a) iii)	<b>One</b> mark for each correct loop <b>max two</b> <div><div>PQ</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>(1)</td><td>0</td><td>0</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>(1)</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>(1)</td><td>0</td></tr><tr><td>10</td><td>(1)</td><td>0</td><td>0</td><td>0</td></tr></table></div>		00	01	11	10	00	(1)	0	0	0	01	0	0	(1)	0	11	0	0	(1)	0	10	(1)	0	0	0	2
	00	01	11	10																							
00	(1)	0	0	0																							
01	0	0	(1)	0																							
11	0	0	(1)	0																							
10	(1)	0	0	0																							
a) iv)	<b>One</b> mark per point • $\bar{P}.\bar{Q}.\bar{S}$ • $+P.Q.S$ $X = \bar{P}.\bar{Q}.\bar{S} + P.Q.S$	2																									
b)	<b>One</b> mark for correct use of distributive law <b>One</b> mark for correct use of complementary law <b>One</b> mark for correct use of redundancy law <b>One</b> mark for correct use of idempotent law <b>Max two</b> $X = \bar{P}.\bar{Q}.\bar{R}.\bar{S} + \bar{P}.\bar{Q}.R.\bar{S} + P.Q.\bar{R}.S + P.Q.R.S$ $X = \bar{P}.\bar{Q}.\bar{S}(\bar{R} + R) + P.Q.S(\bar{R} + R)$ $X = \bar{P}.\bar{Q}.\bar{S} + P.Q.S // \bar{P}.\bar{Q}.\bar{S}(1) + P.Q.S(1)$	2																									

## Question No. 27

a) i)	<b>One</b> mark for 2 correct terms <b>or two</b> marks for 4 correct terms and no other terms $X = \bar{P}.\bar{Q}.\bar{R}.\bar{S} + \bar{P}.Q.\bar{R}.\bar{S} + P.\bar{Q}.R.S + P.Q.R.S$	2																									
a) ii)	<b>Two marks</b> for fully correct K-map <b>One mark</b> for a K-map with one error <b>Zero marks</b> for a K-map with two or more errors <div><div>PQ</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>10</td><td>0</td><td>0</td><td>0</td><td>0</td></tr></table></div>		00	01	11	10	00	1	1	0	0	01	0	0	0	0	11	0	0	1	1	10	0	0	0	0	2
	00	01	11	10																							
00	1	1	0	0																							
01	0	0	0	0																							
11	0	0	1	1																							
10	0	0	0	0																							
a) iii)	<b>One</b> mark for each correct loop <b>max 2</b> <div><div>PQ</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>10</td><td>0</td><td>0</td><td>0</td><td>0</td></tr></table></div>		00	01	11	10	00	1	1	0	0	01	0	0	0	0	11	0	0	1	1	10	0	0	0	0	2
	00	01	11	10																							
00	1	1	0	0																							
01	0	0	0	0																							
11	0	0	1	1																							
10	0	0	0	0																							
a) iv)	<b>One</b> mark per point • $\bar{P}\bar{R}\bar{S}$ • $+P.R.S$ $X = \bar{P}\bar{R}\bar{S} + P.R.S$	2																									
b)	<b>One</b> mark for correct use of distributive law <b>One</b> mark for correct use of complementary law <b>One</b> mark for correct use of redundancy law <b>Max two</b> e.g. $X = \bar{P}.\bar{Q}.\bar{R}.\bar{S} + \bar{P}.Q.\bar{R}.\bar{S} + P.\bar{Q}.R.S + P.Q.R.S$ $X = \bar{P}.\bar{R}.\bar{S}(\bar{Q} + Q) + P.R.S(\bar{Q} + Q)$ $X = \bar{P}\bar{R}\bar{S} + P.R.S \text{ // } \bar{P}.\bar{R}.\bar{S}(1) + P.R.S(1)$	2																									

## Question No. 28

a) i)	<b>One</b> mark for 2 or 3 correct, <b>two</b> marks for 4 correct $X = \bar{P} \cdot \bar{Q} \cdot \bar{R} \cdot \bar{S} + \bar{P} \cdot \bar{Q} \cdot \bar{R} \cdot S + P \cdot Q \cdot R \cdot \bar{S} + P \cdot Q \cdot R \cdot S$	2																																	
a) ii)	<b>One</b> mark for each correct pair of rows/columns to <b>max 2</b>  <table><tr><td colspan="2"></td><th colspan="4">PQ</th></tr><tr><td colspan="2"></td><th>00</th><th>01</th><th>11</th><th>10</th></tr><tr><th rowspan="4">RS</th><th>00</th><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><th>01</th><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><th>11</th><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><th>10</th><td>0</td><td>0</td><td>1</td><td>0</td></tr></table>			PQ						00	01	11	10	RS	00	1	0	0	0	01	1	0	0	0	11	0	0	1	0	10	0	0	1	0	2
		PQ																																	
		00	01	11	10																														
RS	00	1	0	0	0																														
	01	1	0	0	0																														
	11	0	0	1	0																														
	10	0	0	1	0																														
a) iii)	<b>One</b> mark for each correct loop <b>max 2</b>  <table><tr><td colspan="2"></td><th colspan="4">PQ</th></tr><tr><td colspan="2"></td><th>00</th><th>01</th><th>11</th><th>10</th></tr><tr><th rowspan="4">RS</th><th>00</th><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><th>01</th><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><th>11</th><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><th>10</th><td>0</td><td>0</td><td>1</td><td>0</td></tr></table>			PQ						00	01	11	10	RS	00	1	0	0	0	01	1	0	0	0	11	0	0	1	0	10	0	0	1	0	2
		PQ																																	
		00	01	11	10																														
RS	00	1	0	0	0																														
	01	1	0	0	0																														
	11	0	0	1	0																														
	10	0	0	1	0																														
a) iv)	<b>One</b> mark per bullet point • $\bar{P} \cdot \bar{Q} \cdot \bar{R}$ • $+P \cdot Q \cdot R$ $X = \bar{P} \cdot \bar{Q} \cdot \bar{R} + P \cdot Q \cdot R // X = P \cdot Q \cdot R + \bar{P} \cdot \bar{Q} \cdot \bar{R}$	2																																	
b)	<b>One</b> mark for correct use of distributive law <b>One</b> mark for correct use of complement law $X = \bar{P} \cdot \bar{Q} \cdot \bar{R}(\bar{S} + S) + P \cdot Q \cdot R(\bar{S} + S)$ $X = \bar{P} \cdot \bar{Q} \cdot \bar{R}(1) + P \cdot Q \cdot R(1)$  or  <b>Two</b> marks for correct use of redundancy law  $X = (\bar{P} \cdot \bar{Q} \cdot \bar{R}) \cdot \bar{S} + (\bar{P} \cdot \bar{Q} \cdot \bar{R}) \cdot S + (P \cdot Q \cdot R) \cdot \bar{S} + (P \cdot Q \cdot R) \cdot S$ $X = \bar{P} \cdot \bar{Q} \cdot \bar{R} + P \cdot Q \cdot R$	2																																	

## Question No. 29

a) i)	<b>One</b> mark for 2 or 3 correct, 2 marks for 4 correct $X = \bar{P}.\bar{Q}.\bar{R}.\bar{S} + \bar{P}.Q.R.S + P.\bar{Q}.\bar{R}.\bar{S} + P.Q.R.S$	2																																	
a) ii)	<b>One</b> mark two correct rows/columns or <b>Two</b> marks for four correct rows/columns  <table><tr><td colspan="2"></td><th colspan="4">PQ</th></tr><tr><td colspan="2"></td><th>00</th><th>01</th><th>11</th><th>10</th></tr><tr><th rowspan="4">RS</th><th>00</th><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><th>01</th><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><th>11</th><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><th>10</th><td>0</td><td>0</td><td>0</td><td>0</td></tr></table>			PQ						00	01	11	10	RS	00	1	0	0	1	01	0	0	0	0	11	0	1	1	0	10	0	0	0	0	2
		PQ																																	
		00	01	11	10																														
RS	00	1	0	0	1																														
	01	0	0	0	0																														
	11	0	1	1	0																														
	10	0	0	0	0																														
a) iii)	<b>One</b> mark for each correct loop max 2  <table><tr><td colspan="2"></td><th colspan="4">PQ</th></tr><tr><td colspan="2"></td><th>00</th><th>01</th><th>11</th><th>10</th></tr><tr><th rowspan="4">RS</th><th>00</th><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><th>01</th><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><th>11</th><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><th>10</th><td>0</td><td>0</td><td>0</td><td>0</td></tr></table>			PQ						00	01	11	10	RS	00	1	0	0	1	01	0	0	0	0	11	0	1	1	0	10	0	0	0	0	2
		PQ																																	
		00	01	11	10																														
RS	00	1	0	0	1																														
	01	0	0	0	0																														
	11	0	1	1	0																														
	10	0	0	0	0																														
a) iv)	<b>One</b> mark per bullet point • $\bar{Q}.\bar{R}.\bar{S}$ • $+Q.R.S$ $X = \bar{Q}.\bar{R}.\bar{S} + Q.R.S$ or $X = Q.R.S + \bar{Q}.\bar{R}.\bar{S}$	2																																	
b)	<b>One</b> mark for correct use of distributive law <b>One</b> mark for correct use of complement law  $X = \bar{Q}.\bar{R}.\bar{S}(\bar{P} + P) + Q.R.S(\bar{P} + P)$ $X = \bar{Q}.\bar{R}.\bar{S}(1) + Q.R.S(1)$  Or  Two marks for correct use of redundancy law  $X = (\bar{Q}.\bar{R}.\bar{S})\bar{P} + (\bar{Q}.\bar{R}.\bar{S})P + (Q.R.S)\bar{P} + (Q.R.S)P$  $X = \bar{Q}.\bar{R}.\bar{S} + Q.R.S$	2																																	

## Question No. 30

A	<p>One mark per two correct products (Max 3)</p> <p><math>(Z =) A \bar{B} \bar{C} D + A \bar{B} C D + A B \bar{C} \bar{D} + A B \bar{C} D +</math> <math>A B C \bar{D} + A B C D</math></p>	3																									
b) i)	<p>One mark for every two correct rows or columns (Max 2)</p> <p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>10</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table> <p style="text-align: center;">CD</p>		00	01	11	10	00	0	0	1	0	01	0	0	1	1	11	0	0	1	1	10	0	0	1	0	2
	00	01	11	10																							
00	0	0	1	0																							
01	0	0	1	1																							
11	0	0	1	1																							
10	0	0	1	0																							
b) ii)	<p>One mark for correct loop (Max 2)</p> <p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>10</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table> <p style="text-align: center;">CD</p>		00	01	11	10	00	0	0	1	0	01	0	0	1	1	11	0	0	1	1	10	0	0	1	0	2
	00	01	11	10																							
00	0	0	1	0																							
01	0	0	1	1																							
11	0	0	1	1																							
10	0	0	1	0																							
b) iii)	<p>One mark per correct marking point (Max 2)</p> <ul style="list-style-type: none"><li>• <math>A B // A D</math></li><li>• <math>+ A D // + A B</math></li></ul> <p><math>(Z =) A B + A D // A D + A B</math></p>	2																									
b) iv)	<p><math>(Z =) A (B + D) // A (D + B)</math></p>	1																									